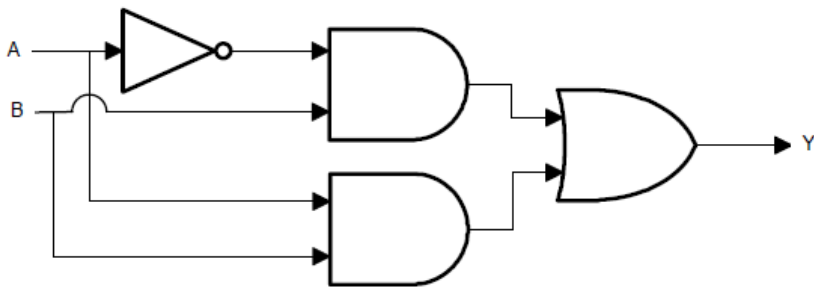





**Sri Lanka Institute of Information Technology**  
**B. Sc Degree in IT/IS/CSN, Diploma in Information Technology**  
**Year 01 – Semester I – 2017**  
**Mathematics for Computing (IT1030)**  
**Tutorial 01**


1. Draw a truth table for a three input AND gate and a FOUR input OR gate.
2. Find the outputs of the following circuits.
  - a.



b.

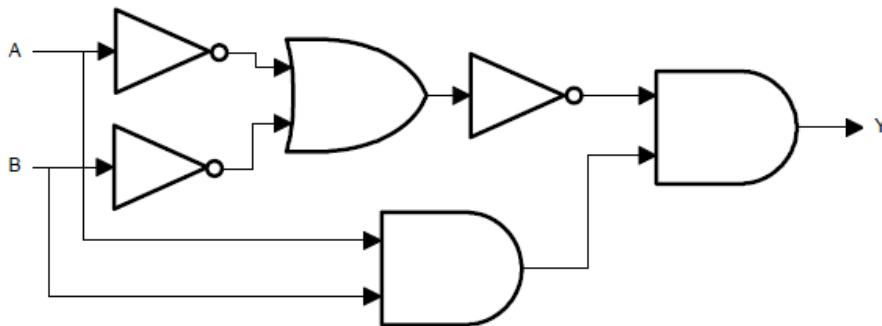

c.

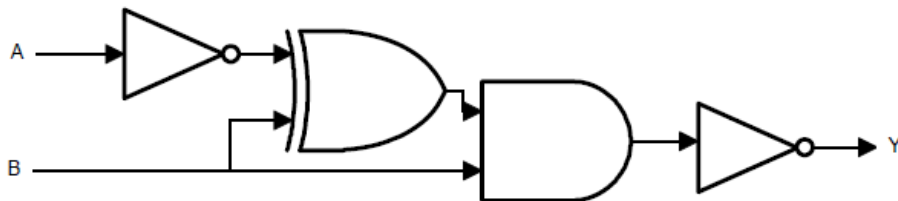

3. What type of logic gate's behavior does this truth table represent?

?			
A	B	C	?
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

- I. 2 input OR
  - II. 3 input OR
  - III. 3 input EXOR
  - IV. 4 input EXOR
4. A nuclear power station has a safety system based on three inputs to a logic circuit (network). A warning signal ( $S = 1$ ) is produced when certain conditions in the nuclear power station occur based on these three inputs.

Inputs	Binary values	Description of plant status
<b>T</b>	1	Temperature > 115°C
	0	Temperature <= 115°C
<b>P</b>	1	Reactor pressure > 15 bar
	0	Reactor pressure <= 15 bar
<b>W</b>	1	Cooling water > 120 litres/hour
	0	Cooling water <= 120 litres/hour

A warning signal ( $S = 1$ ) will be produced when any of the following occurs:

- (a) Temperature > 115°C and Cooling water <= 120 litres/ hour
- or
- (b) Temperature <= 115°C and Reactor pressure > 15 bar
- or
- (c) Cooling water <= 120 litres/hour

Draw a logic circuit (network) and truth table to show all the possible situations when the warning signal ( $S$ ) could be received.